
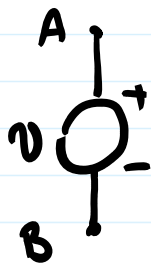


for a wire:  $R = \rho \frac{l}{A}$

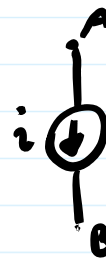$\rho$  → Resistivity of material  
 $l$  → length  
 $A$  → cross-sectional area




voltage source:  
 $V = V_A - V_B$



current source  
 $i_{AB} = i$  (given)


Power dissipation in resistor:  $P = Ri^2 = \frac{V^2}{R}$

Ideal capacitor:

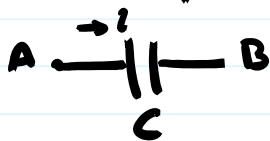

$q = C(V_A - V_B)$  or  $q = CV$

$q$  → charge  
 $C$  → capacitance

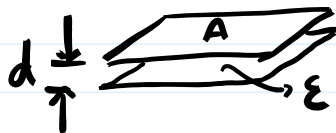

$C = \frac{\epsilon A}{d}$


$\epsilon$  → dielectric const.  
 $A$  → Area of flat plates  
 $d$  → distance of the plates.

$$i = \frac{dq}{dt} = C \frac{dV}{dt} \Rightarrow dV = \frac{1}{C} i dt$$

$$\text{or } V = V_0 + \frac{1}{C} \int_0^t i dt$$

Stored energy in capacitor:  $w = \frac{1}{2} CV^2$

## \* Inductor.

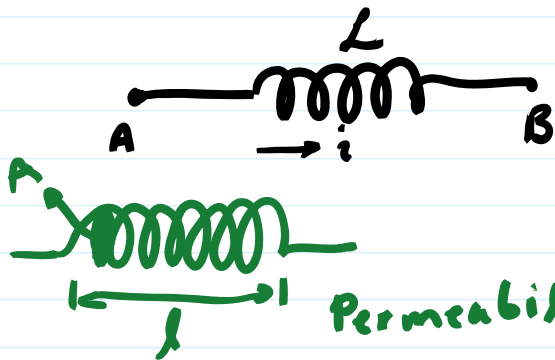

$$V_A - V_B = L \frac{di}{dt} \quad [H]$$

$$L = \frac{\mu \overset{\text{\# of turns}}{N^2} \overset{\text{Cross-sectional area}}{A}}{\underset{\text{length}}{l}}$$

## \* Kirchhoff's Current Law (KCL):


Sum of the currents entering a node is equal to sum of currents leaving that node



$$i_1 = i_2 + i_3$$

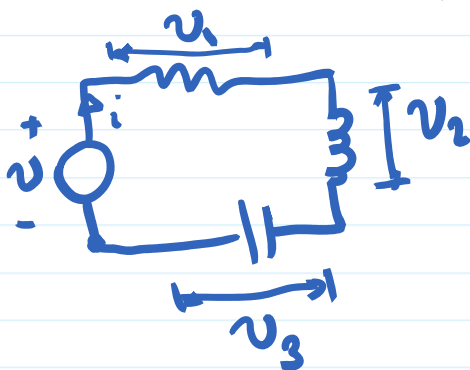
## \* Kirchhoff's Voltage Law (KVL).

Sum of all the voltage changes around a complete loop is zero



$$v - v_1 - v_2 - v_3 = 0$$

\* RLC circuit.

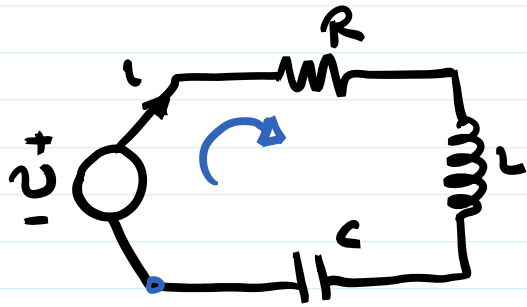

$$\text{KVL: } v - iR - L \frac{di}{dt} - \frac{1}{C} \int i dt = 0$$

$$L \frac{di}{dt} + Ri + \underbrace{\frac{1}{C} \int i dt}_q = v$$


$$\text{if } q = \int i dt \quad i = \dot{q} \quad \frac{di}{dt} = \ddot{q}$$

$$\Rightarrow \boxed{L \ddot{q} + R \dot{q} + \frac{1}{C} q = v}$$

Standard second order oscillator

$$m \ddot{x} + c \dot{x} + kx = f$$

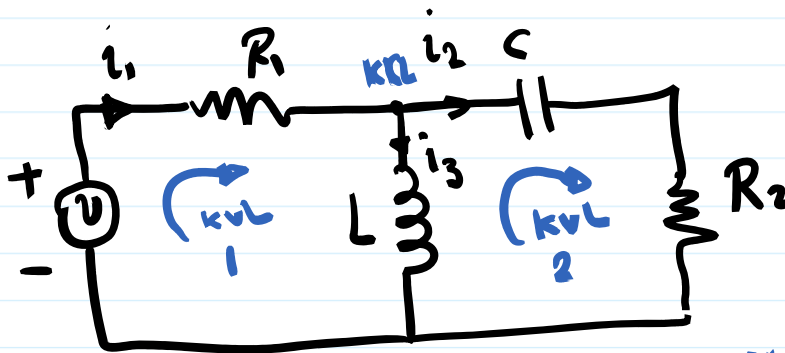$\downarrow$   $\downarrow$   $\downarrow$   
 $L$   $R$   $1/C$   
 inertia element      damping      Spring Constant or energy storage element.




$$\text{KVL 1: } v - i_1 R_1 - L \frac{di_3}{dt} = 0$$

$$\text{KVL 2: } -\frac{1}{C} \int i_2 dt - R_2 i_2 + L \frac{di_3}{dt} = 0$$

$$\text{KCL: } i_1 = i_2 + i_3$$

Let's replace  $i_3$  by  $i - i_2$
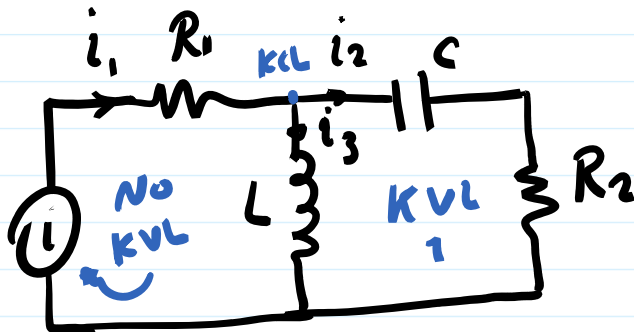
$$\begin{cases} L \frac{di_1}{dt} - L \frac{di_2}{dt} + R_1 i_1 = V \\ L \frac{di_2}{dt} - L \frac{di_1}{dt} + R_2 i_2 + \frac{1}{C} \int i_2 dt = 0 \end{cases}$$



KCL:  $i_1 = i_2 + i_3$   
 $i = i_2 + i_3$   
 $i_3 = i - i_2$



$$-\frac{1}{C} \int i_2 dt - i_2 R_2 + L \frac{d(i - i_2)}{dt} = 0$$

or.  $L \frac{di_2}{dt} + R_2 i_2 + \frac{1}{C} \int i_2 dt = \underbrace{L \frac{di}{dt}}_{\text{input}}$

Series and parallel Resistors/Capacitors/Inductors:

Series

$\begin{array}{c} \text{---} R_1 \text{---} R_2 \text{---} \\ \text{---} L_1 \text{---} L_2 \text{---} \\ \text{---} C_1 \text{---} C_2 \text{---} \end{array}$	$\equiv$	$\begin{array}{c} \text{---} R_{eq} \text{---} \\ \text{---} L_{eq} \text{---} \\ \text{---} C_{eq} \text{---} \end{array}$	$R_{eq} = R_1 + R_2$
			$L_{eq} = L_1 + L_2$
			$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$

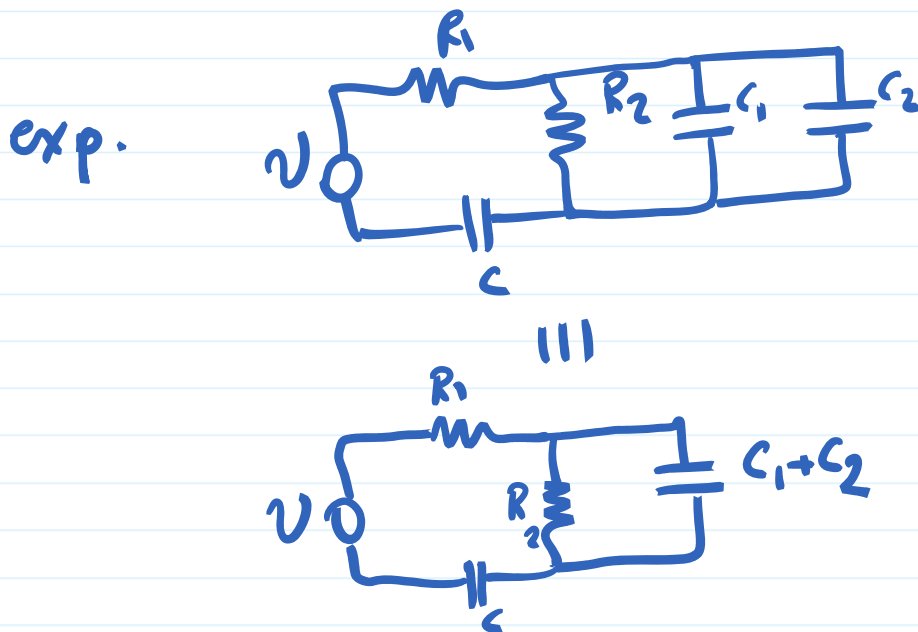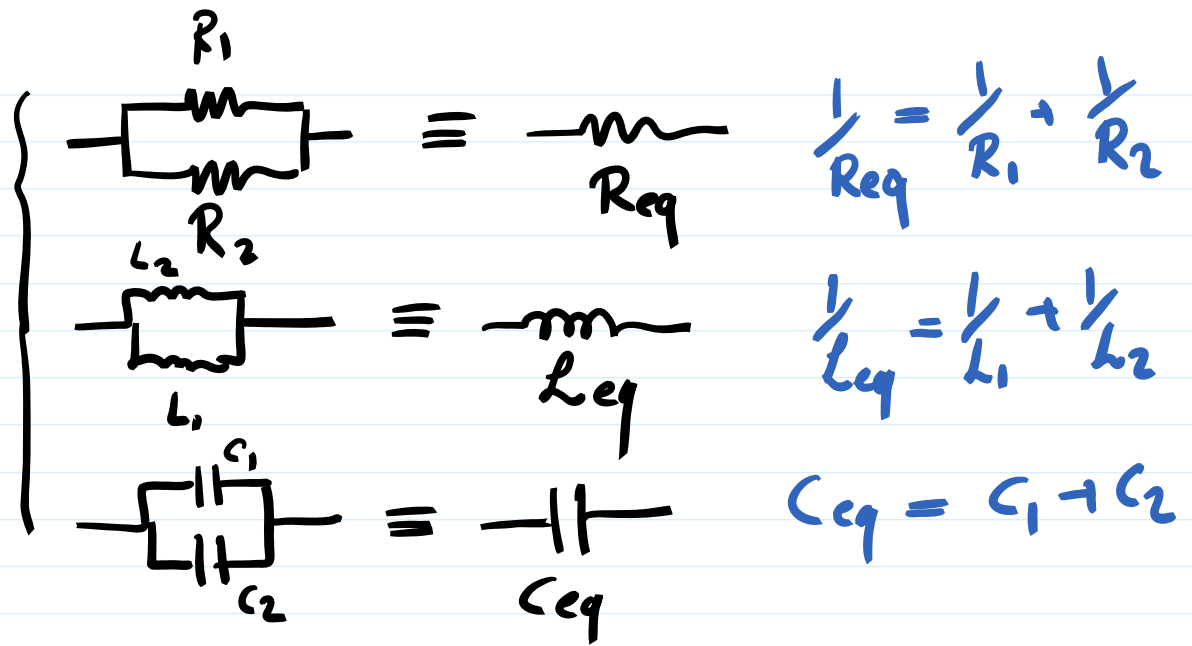

Simplify first, then write the KVL & KCL equations